



Exam 2013, questions and answers

Principles of Electrical Engineering (Concordia University)




Scan to open on Studocu

Elec-275: Winter 2013 Final Exam Solution

1. (a) For the time-domain circuit of Fig. 1, draw its phasor domain circuit. [Designate I_1 , I_2 , and V as the phasors of $i_1(t)$, $i_2(t)$, and $v(t)$ respectively]. Draw this phasor circuit.
- (b) Using **mesh analysis** on this phasor circuit, determine I_2 and V . Use the meshes shown.
- (c) Then write the time domain expressions of $i_2(t)$ and $v(t)$.

Solution:

(a) Phasor circuit:

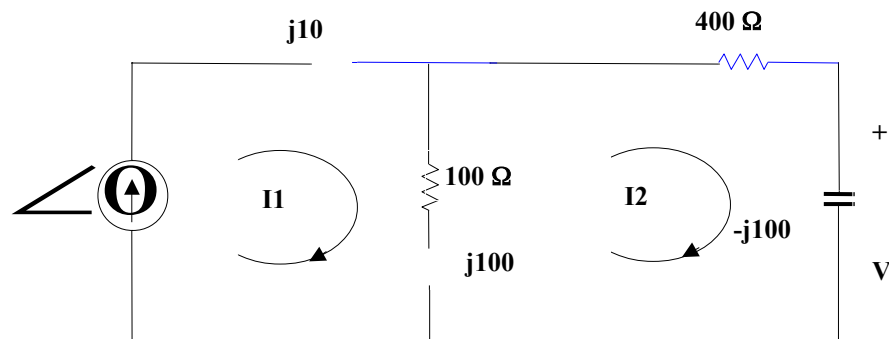

(b) $I_1 = 0.5 \angle 0^\circ$

$$\text{KVL: } 500 I_2 - (100 + j100) I_1 = 0; \text{ or } 500 I_2 = (100 + j100) \cdot 0.5 \angle 0^\circ = 50 + j50.$$

$$\text{or } I_2 = 0.1 + j0.1 = 0.1414 \angle 45^\circ; \quad V_2 = -j100 I_2 = 14.14 \angle -45^\circ.$$

(c) $i_2(t) = 0.1414 \cos(1000t + 45^\circ)$ amps; $v_2(t) = 14.14 \cos(1000t - 45^\circ)$ volts.

2. Using **nodal analysis** in the phasor circuit of Fig.2,

(a) determine the voltages V_2 , V_3 , and the current I ;

(b) draw the phasor diagrams (plot of phasors in the complex plane) of V_1 , V_2 , V_3 , and I .

Solution:

(a) KCL @ V_2 : $\frac{V_2 - 10 \angle 0^\circ}{10 \Omega} + \frac{V_2 - V_3}{j20 \Omega} + \frac{V_2}{-j10 \Omega} = 0$; or $(-1 + j2)V_2 + 2V_3 = 2 \angle 30^\circ \dots (1)$

KCL @ V_3 : $\frac{V_3}{j10 \Omega} + \frac{V_3}{5 \Omega} + \frac{V_3 - V_2}{-j10 \Omega} - 2 \angle 30^\circ = 0$; or $V_2 + j2V_3 = -10 + j17.32 \dots (2)$


volts **amps**

From (1) and (2): $V_2 = 6.33 \angle 41.6^\circ$; $V_3 = 5.3 \angle 24.2^\circ$; $I = V_2/(j20) = 0.3165 \angle -$
48.4

(b) Phasor diagrams may now be drawn.


3. (a) Replace the circuit to the left of **a - b** of Fig. 3 by its **Thevenin** equivalent. Draw this equivalent circuit.

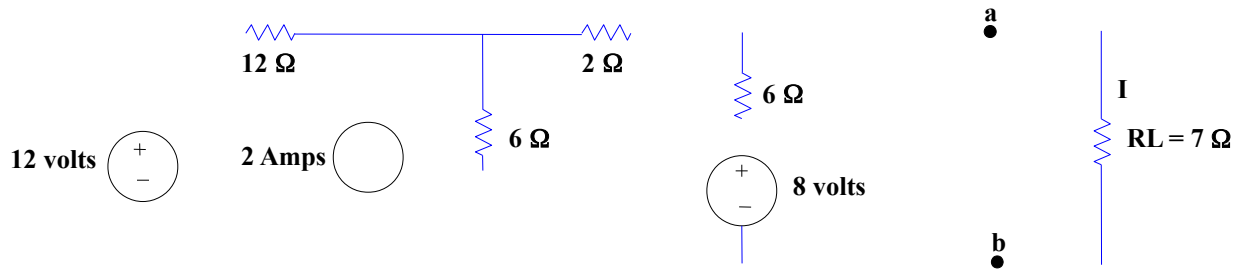(b) Using this equivalent circuits, determine the current **I** through the load resistor R_L .



Solution:

V_{th} :

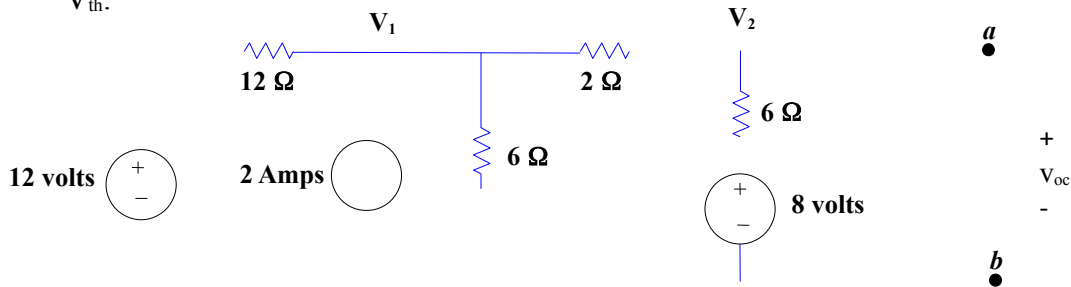


$$\text{KCL @ } V_1: \frac{V_1 - 12}{12} - 2 + \frac{V_1}{6} + \frac{V_1 - V_2}{2} = 0 \quad ; \quad \text{or} \quad 9V_1 - 6V_2 = 36 \quad \dots (1)$$

$$\text{KCL @ } V_2: \frac{V_2 - V_1}{2} + \frac{V_2 - 8}{6} = 0 \quad ; \quad \text{or} \quad -3V_1 + 4V_2 = 8 \quad \dots (2).$$

From (1) and (2), $V_2 = V_{th} = 10$ volts.

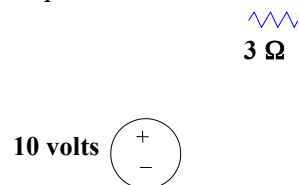$R_{th} = 3 \Omega$. Thevenin equivalent:




(b) $I = 1$ A.


4. An ideal transformer with a turns ratio of **N** in Fig. 4 is used to match the load Z_L for maximum power transfer. For that purpose, determine:

(a) the transformer turns ratio;

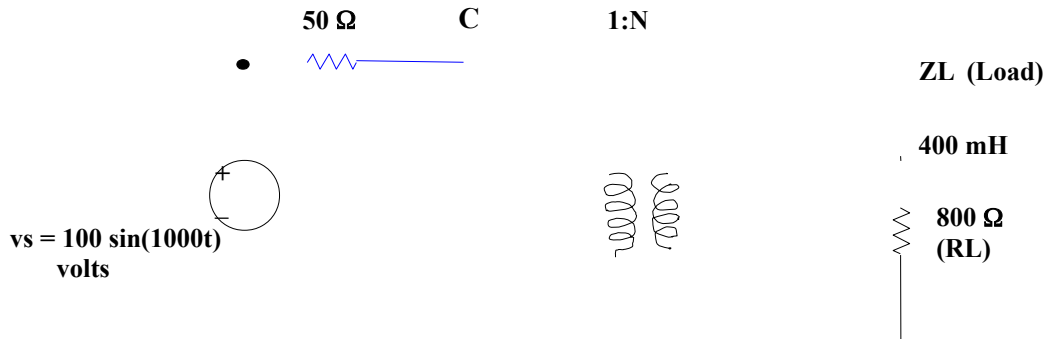- (b) the value of the capacitor C ;
 (c) the power absorbed by the load.




Solution:

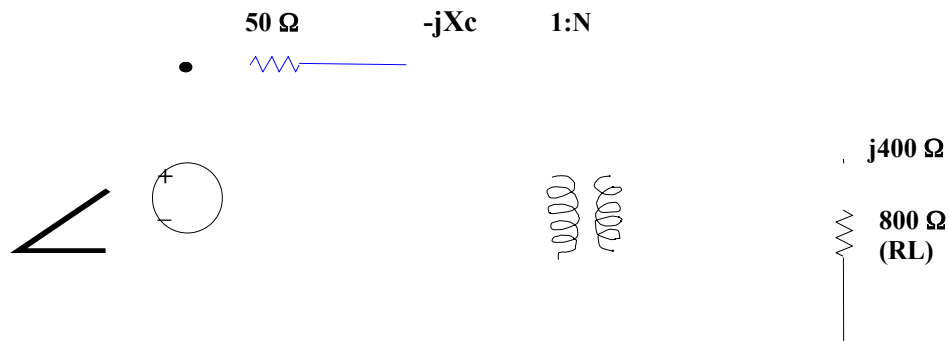

$$\begin{aligned} \text{(a): } N^2 &= \frac{800}{50} = 16 \quad ; \quad N = 4. \\ \text{(b) } X_c &= \frac{400}{16} = 25 = \frac{1}{1000 \times C} \quad ; \quad C = 40 \mu\text{F}. \\ \text{(c) } P &= \frac{\left(\frac{50}{\sqrt{2}}\right)^2}{50} = 25 \text{ watts.} \end{aligned}$$

5. A three-phase 60 Hz power supply is connected to a three-phase motor as shown in Fig. 5. Find:

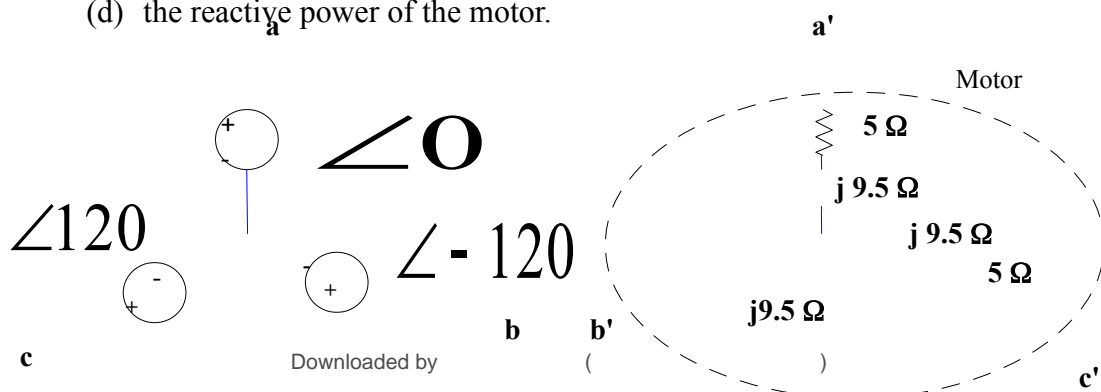- (a) the power factor
 (b) the apparent power of the motor
 (c) the real power of the motor
 (d) the reactive power of the motor.



Solution:

Using single phase circuit: $Z_L = 5 + j9.5 = 10.735 \angle 62.24$

(a) **P.F.** = $\cos 62.24 = 0.4657$.

$$(b) \quad S = \frac{V_{rms}^2}{Z^*} = \frac{120^2}{10.735 \angle -62.24} = 1341.4 \angle 62.24 = 624.7 + j 1187$$

Total power = $3 S = 4024.2 \angle 62.24$
Apparent power = 4024.2 VA

(c) **Real power** = 1874.34 W

(d) **Reactive power** = 3561 VAR.

6. For the magnetic circuit of Fig.6:

- Air gap cross sectional area = 2 cm \times 2 cm (for both gaps)
- Air gap lengths:

$$l_{g1} = 2 \text{ mm}$$

$$l_{g2} = 4 \text{ mm}$$
- Neglect the reluctance of the magnetic metallic structure (compared to those of the air gaps), as well as the fringing effect.
- The magnetizing coil has 100 turns and carries a current of 0.5 amps.

(a) Determine, for each air gap:

- (i) the reluctance **R**;
- (ii) the flux **ϕ** .

(b) Find

- (i) the flux density **B** for air gap-1 only;
- (ii) the field intensity **H** for air gap-1 only.

(c) Find the equivalent reluctance seen by the magnetomotive force **NI**.

Solution:

$$A = 4 \times 10^{-4} \text{ m}^2.$$

$$(a) \quad \text{Air gap 1:} \quad (i) \quad \mathbf{R}_1 = \frac{2 \times 10^{-3}}{4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 3.98 \times 10^6 \quad \text{A-turns/Wb;}$$

$$(ii) \quad \phi_1 = \frac{NI}{R_1} = \frac{50}{3.98 \times 10^6} = 12.566 \times 10^{-6} \quad \text{Wb.}$$

$$\text{Air gap 2:} \quad (i) \quad \mathbf{R}_2 = 7.98 \times 10^6 \quad \text{A-turns/Wb;}$$

$$(ii) \quad \phi_2 = 6.283 \times 10^{-6} \quad \text{Wb.}$$

$$(b) \quad (i) \quad \mathbf{B} = \frac{\phi_1}{A} = \frac{12.566 \times 10^{-6}}{4 \times 10^{-4}} = 0.0314 \quad \text{Wb/m}^2$$

$$(ii) \quad \mathbf{H} = \frac{B}{\mu_0} = \frac{0.0314}{4\pi \times 10^{-7}} = 25 \times 10^3 \quad \text{A-turn/m.}$$

$$(c) \quad R_{eq} = R_1 \parallel R_2 = 2.65 \quad \text{A-turn/Wb.}$$

$$7. \quad (a) \quad I_f = 240/120 = 2 \quad \text{A.}$$

$$\text{At no-load: } I_a = 6 - 2 = 4 \text{ A.} \quad E_b = 240 - 0.4 \times 4 = 238.4 = (K_a \phi) \omega_m$$

$$= K_a \phi \times \frac{2000}{60} \times 2\pi; \quad \text{or } K_a \phi = \frac{238.4}{2000 \times 2\pi} \times 60 = 1.138.$$

$$(b) \quad \text{At full-load: } I_a = 50 - 2 = 48 \text{ amps; } E_b = 240 - 48 \times 0.4 = 220.8 \text{ volts.}$$

$$(c) \quad \text{Speed} = \omega_m = \frac{220.8}{1.138} \times \frac{60}{2\pi} = 1852.35 \quad \text{rpm.}$$

$$(d) \quad \text{Torque} = (K_a \phi) I_a = 1.138 \times 48 = 54.637 \quad \text{N-m}$$

$$(e) \quad \text{Power} = \text{Torque} \times \text{speed} = 54.637 \times \frac{1852.35}{60} \times 2\pi = 10,598.4 \text{ W} = 14.2 \text{ HP.}$$