



Week 5 Midterm Review ELEC275 annotated

Principles of Electrical Engineering (Concordia University)



Scan to open on Studocu

Midterm review

MIDTERM

WHEN: WEDNESDAY FEB 19th

TIME: 6-8 PM (2 hours)

ROOMS:


Abdouraz – Mohamed FG B050

Moreau – Znaty FG B055

ACSD students will write at the ACSD center

Note: Ensure you go to the right room or you will not be able to write. Bring 1) ENCS approved calculator, 2) student ID, 3) Pen (no pencil). This is a CLOSED book exam with NO formula sheet.

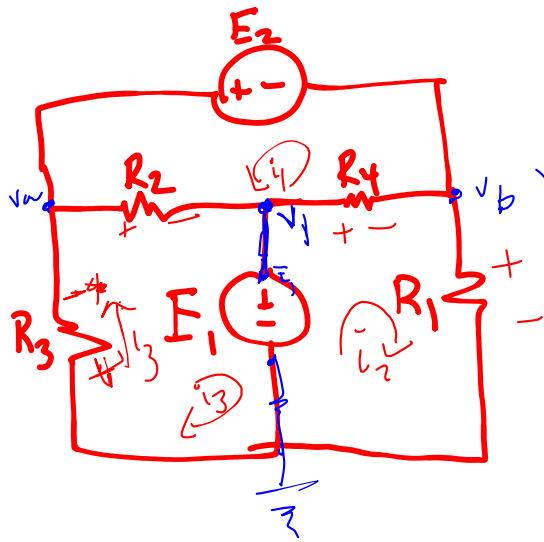Example M1 - Use **mesh analysis** technique to calculate the current through resistance R_3 and identify the direction of the flow. If $E_1 = 6V$, $E_2 = 6V$, $R_1 = 4 \Omega$, $R_2 = 8 \Omega$, $R_3 = 2 \Omega$, $R_4 = 1 \Omega$




$$\text{Mesh 1: } -v_2 + (i_1 + i_3)R_2 + (i_1 + i_2)R_4 = 0$$

$$\text{Mesh 2: } -v_1 + (i_1 + i_2)R_4 + i_2R_1 = 0$$


$$\text{Mesh 3: } i_3R_3 + (i_3 + i_1)R_2 + v_1 = 0$$

Example M2

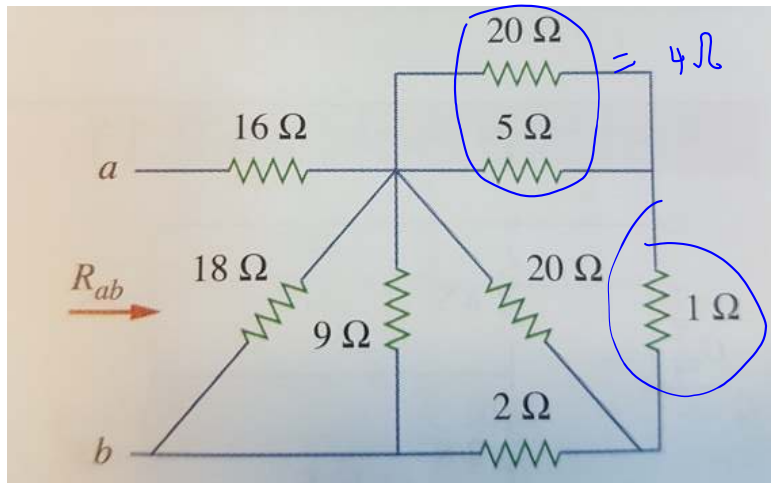


What is R_{ab} between terminals a and b?
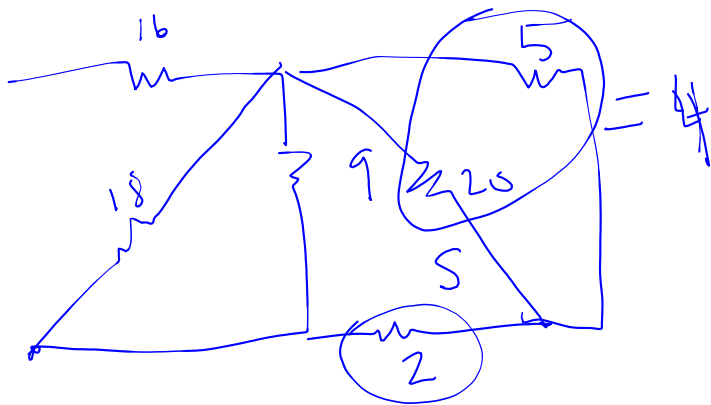
$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




\Rightarrow

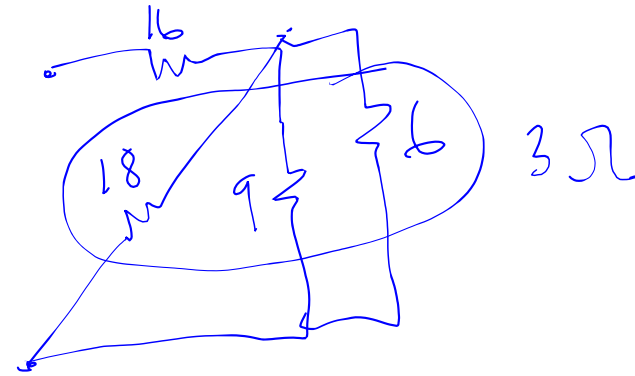

$$R_{eq} = 19 \Omega$$

Example M3

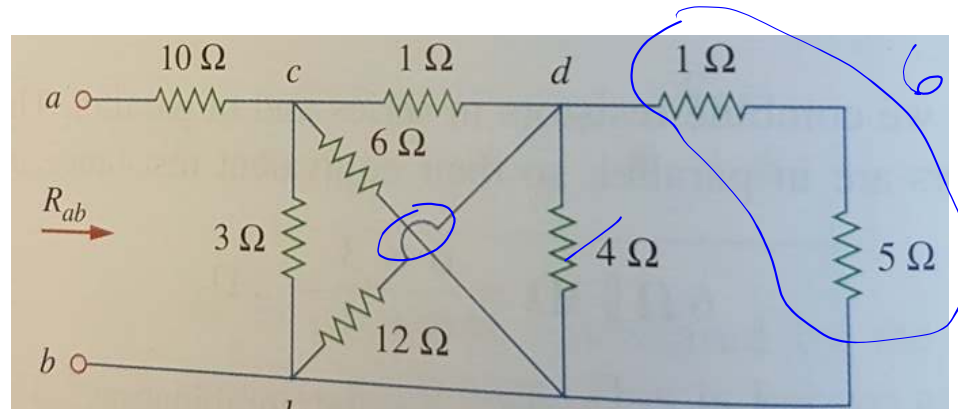

What is R_{ab} between terminals a and b?

$$1. \quad 6 \parallel 4 = \frac{6 \times 4}{6 + 4} = 2.4 \Omega$$




$$2. \quad 2.4 \parallel 4 = 2 \Omega$$

$$3. \quad 2 + 1 = 3 \Omega$$

$$4. \quad 3 \parallel 6 \parallel 4 \parallel 3 = 1.2 \Omega$$

$$5. \quad 1.2 + 10 = \underline{11.2 \Omega}$$

Example M4

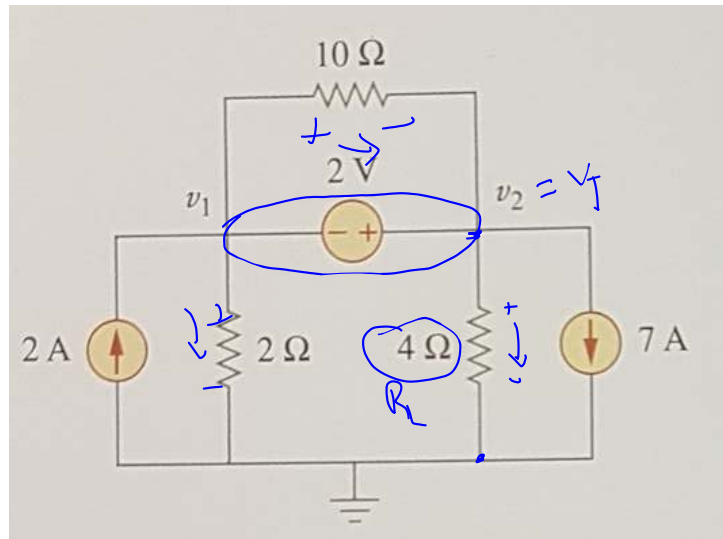

Find v_1 and v_2 .

Find the maximum power delivered to the load if the load is placed between v_2 and ground?


Current away is \oplus $v_2 - v_1 = 2$

$$-2 + \frac{v_1}{2} + \frac{v_2}{4} + 7 = 0$$

$$v_1 = -7.33 \text{ V}$$

$$v_2 = -5.33 \text{ V}$$

Example M4

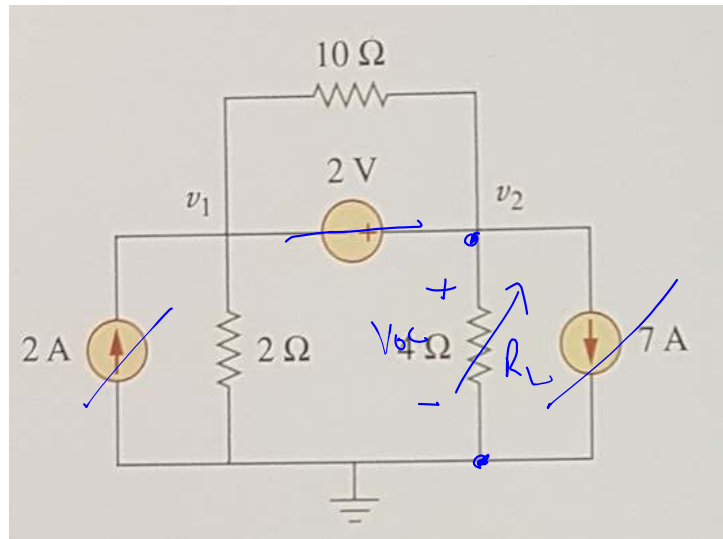

Find v_1 and v_2 .

Find the maximum power delivered to the load if the load is placed between v_2 and ground?

$$R_{eq} = 2\Omega$$


$$P_{max} = \frac{V_{oc}^2}{4R_T}$$

$$-2 + \frac{v_1}{2} + 7 = 0$$

$$v_2 - v_1 = 2$$

$$v_2 = ?$$

Example M5

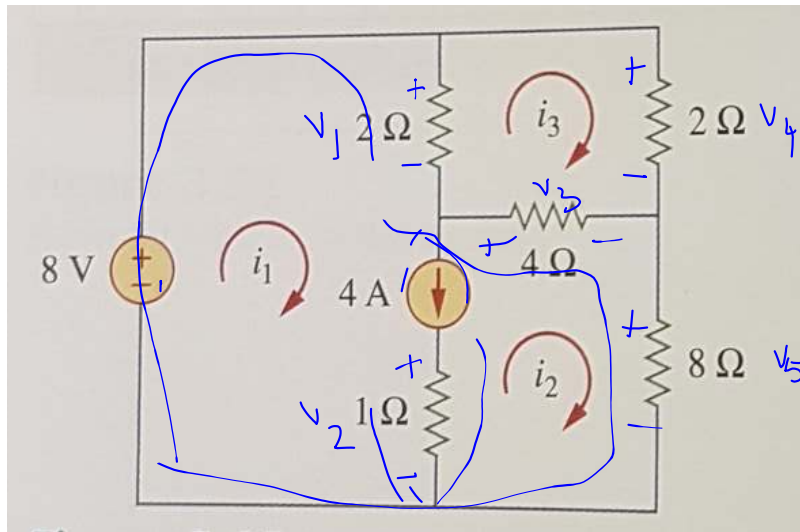

What is i_1 , i_2 , and i_3 ?

Find the maximum power delivered to the load if the load replaces the 8 ohm resistor.

$$\textcircled{1} i_1 - i_2 = 4$$

$$\textcircled{1} v_4 - v_3 - v_1 = 0$$

$$2i_3 - 4(i_2 - i_3) - 2(i_1 - i_3) = 0$$

supermesh

$\textcircled{2}$


$$-8 + v_1 + v_3 + v_5 = 0$$

$$-8 + 2(i_1 - i_3) + 4(i_2 - i_3) + 8i_2 = 0$$

$$i_1 = 4.63 \text{ A}, \quad i_2 = 631.6 \text{ mA}$$


$$i_3 = 1.47 \text{ A}$$

Example M5

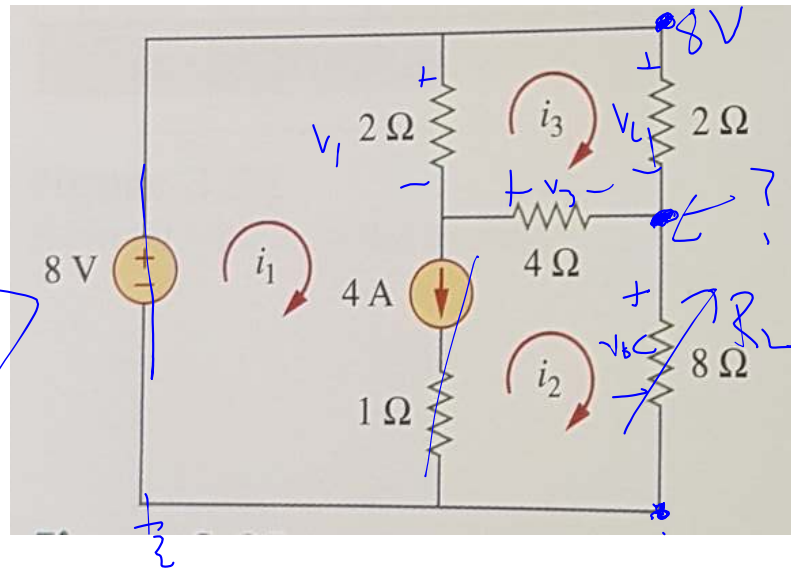

No current source – what Req?
+ short V_{source}
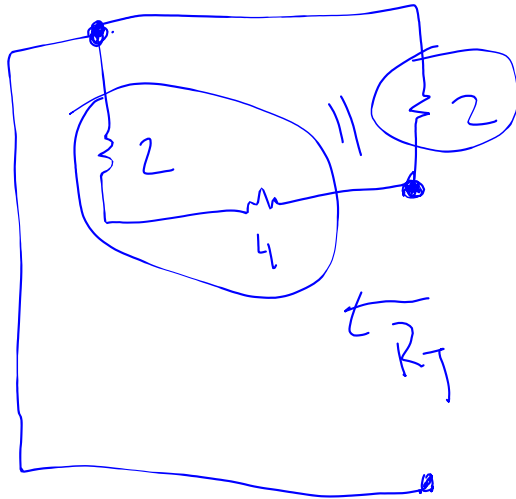
$$R_{eq} = R_T = (4+2) \parallel 2 = 1.5 \Omega$$




$$i_1 = 4A$$

$$\text{Mesh 3: } v_4 - v_3 - v_1 = 0$$


$$2i_3 - 4(-i_3) - 2(i_1 - i_3) = 0$$

$$\hat{i}_3 = 1A$$
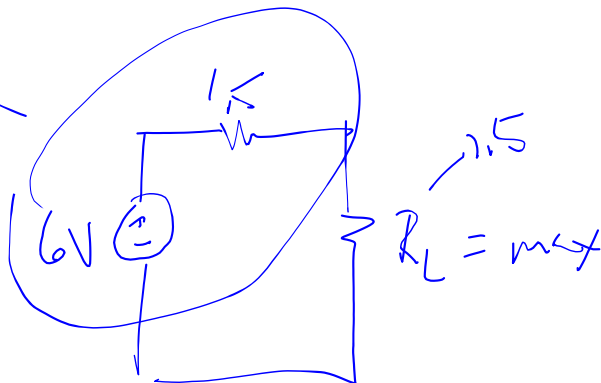
$$\begin{aligned} V_{OC} &= 8 - v_4 \\ &= 8 - 2 \times i_3 = 6V \end{aligned}$$



Example M6

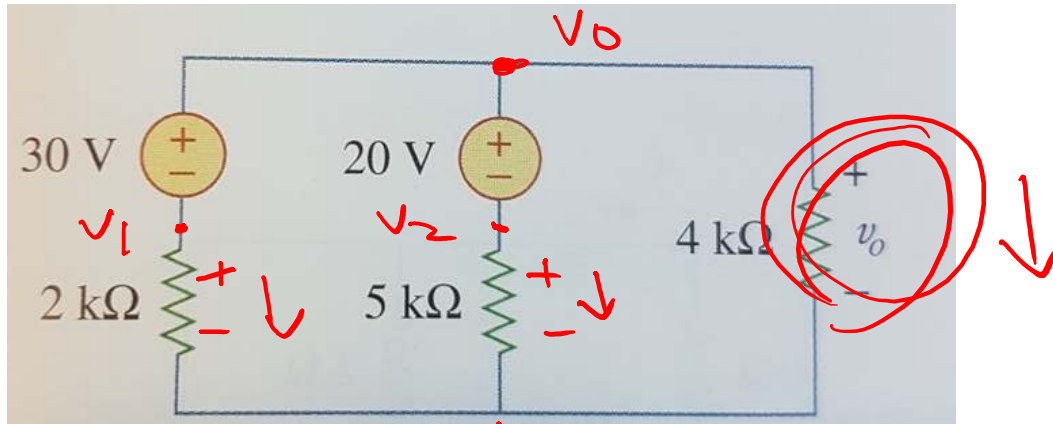

① $v_0 - v_1 = 30 \xrightarrow{+} v_0 - 30 = v_1$ away is +


$$\textcircled{2} \quad v_0 - v_2 = 20 \Rightarrow v_0 - 20 = v_2$$

$$\textcircled{3} \quad \frac{V_1}{2} + \frac{V_2}{5} + \frac{V_0}{4} = 0$$

$$V_0 = 20V$$

current
away is
'+'
+

Example M6

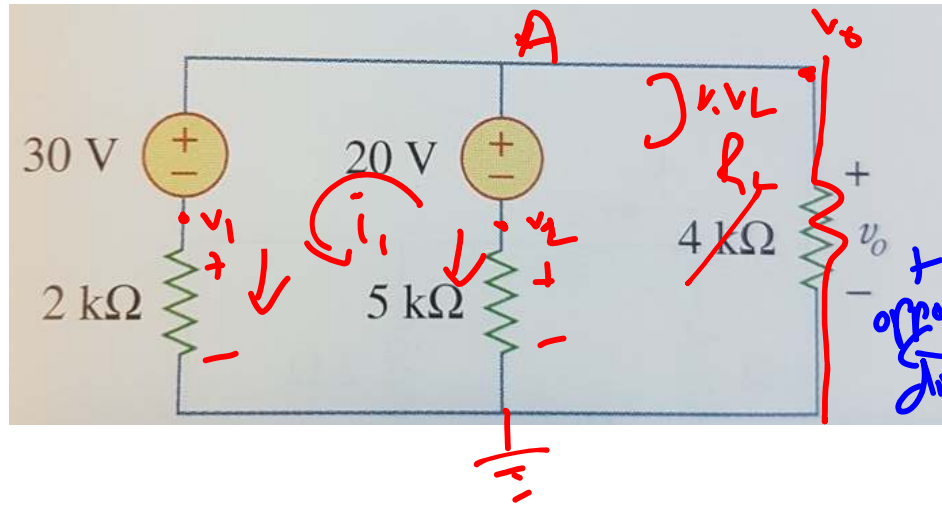

What is V_o for this circuit?

Assume the load is placed at the 4kΩ, what is the Thevenin voltage?

$$R_T = 5 \parallel 2 = 1.43 \Omega$$

$$V_o = V_T$$

$$\textcircled{1} V_o - V_1 = 30$$

$$\textcircled{2} V_o - V_2 = 20$$

$$\textcircled{3} \text{ at A } \rightarrow \frac{V_1}{2} + \frac{V_2}{5k\Omega} = 0$$

$$\frac{V_o - 30}{2} + \frac{V_o - 20}{5} = \frac{V_o}{2} + \frac{V_o}{5} - 15 - 4 = 0$$

$$\text{KVL} \quad +V_o - V_2 - 20 = 0$$

$$V_o = V_2 + 20 = (1.42)(5) + 20 = 27.1V$$

$$\text{mesh} \quad +30 + V_1 - V_2 - 20 = 0$$

$$30 + i_1(2) - (-i_1)(5) - 20 = 0$$


$$7i_1 = -10$$

$$i_1 = -1.42A$$

$$0.7V_o = 19$$

$$V_o = 27.14V$$

Example M7

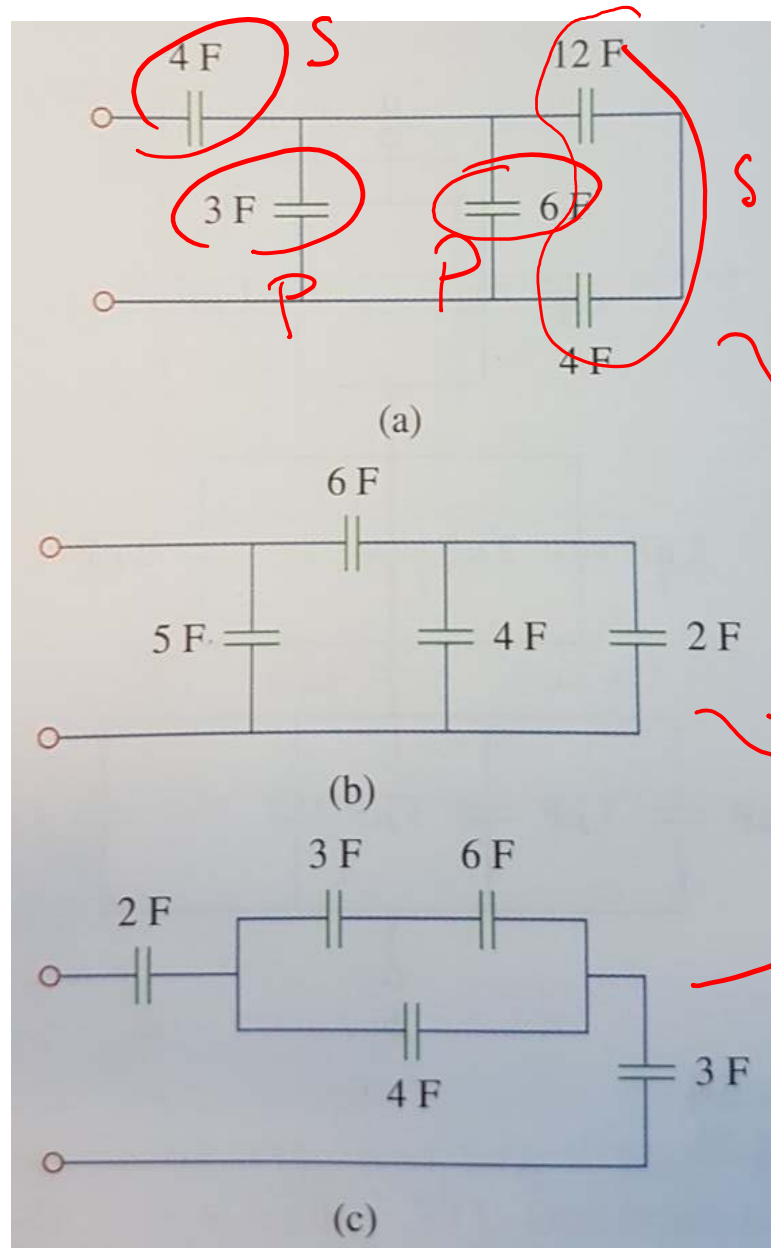

Series Parallel

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)^{-1} \quad C_{eq} = C_1 + C_2 + \dots + C_n$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$


$\rightarrow C_{eq} = 3F$

$$Z_{eq} = \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_n} \right]^{-1}$$

$\rightarrow C_{eq} = 8F$

$\rightarrow 1F$

Example M8

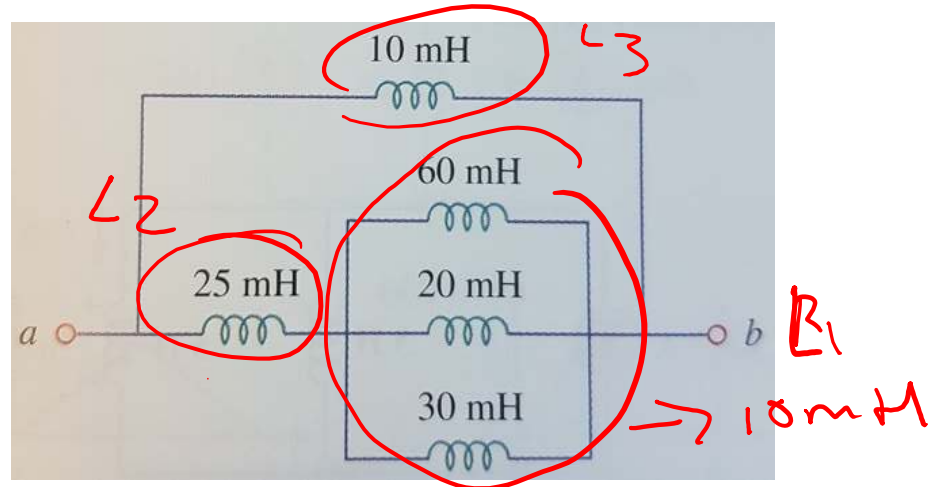

Series

$$L_{eq} = L_1 + L_2 + L_3 + \dots + L_n$$

$$Z_{eq} = Z_1 + Z_2 + \dots + Z_n$$

Parallel

$$L_{eq} = \left[\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \right]^{-1}$$


$$Z_{eq} = \left[\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} \right]^{-1}$$

$$L_1 + L_2 = 35 \text{ mH}$$

$$L_3 \parallel (L_1 + L_2) = 7.78 \text{ mH}$$

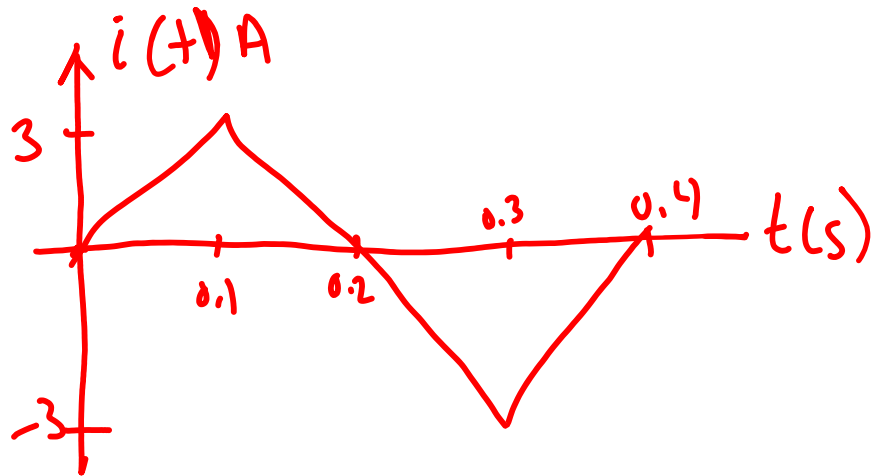Example M9

The current flowing through a 2-H inductance is shown below. Sketch the voltage, power, and stored energy versus time.



$$v(t) = L \frac{di}{dt}$$


$$p(t) = v(t) \cdot i(t)$$

$$= 1800t \quad 0 \leq t < 0.1$$

$$i(t) = \begin{cases} 30t & 0 \leq t < 0.1 \\ -30t + 6 & 0.1 \leq t < 0.2 \\ -30t + 6 & 0.2 \leq t < 0.3 \\ 30t - 12 & 0.3 \leq t < 0.4 \end{cases}$$

$$W(t) = \frac{1}{2} L i(t)^2$$


$$= \frac{1}{2} (2) (30t)^2$$

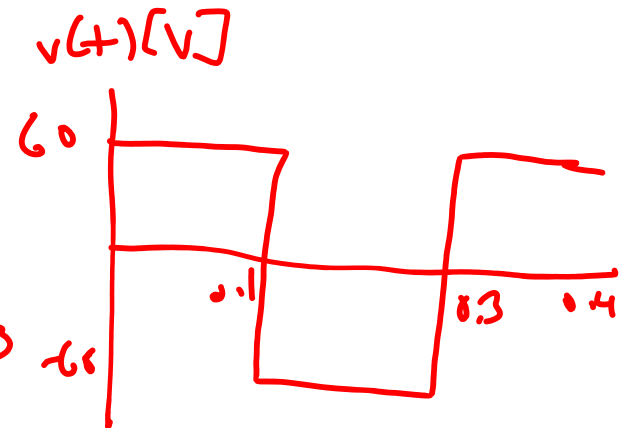

$$v(t) = \begin{cases} 2 \times 30 = 60 \text{ V} & 0 \leq t < 0.1 \\ 2 \times -30 = -60 \text{ V} & 0.1 \leq t < 0.3 \\ 2 \times 30 = 60 \text{ V} & 0.3 \leq t < 0.4 \end{cases}$$

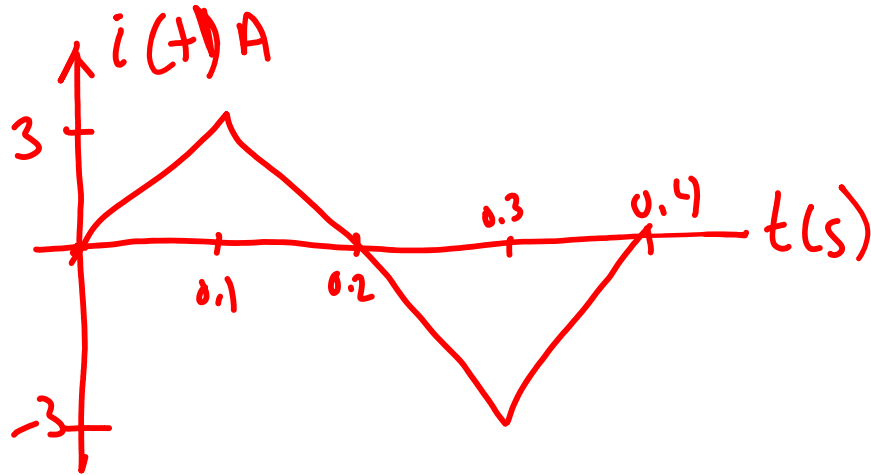Example M9

The current flowing through a 2-H inductance is shown below. Sketch the voltage, power, and stored energy versus time.



$$W(t) = \frac{1}{2} L i(t)^2$$

$$w(t) = i(t)^2$$

$$= (30t)^2 = 900t^2$$

$$= (-30t + 6)^2 = 900t^2 - 360t + 36$$

$$= (30t - 12)^2 = 900t^2 - 720t + 144$$

