



2016 Winter - Exam/Practice

System Hardware (Concordia University)



Scan to open on Studocu

Instructor: Tadeusz Obuchowicz

Date: Tuesday, March 1, 2016

Instructions: Answer all 4 questions in the answer booklets provided.

Time Allowed: up to 2 hours.

Materials Allowed: Any computer organization hardcopy textbook, course lecture notes in hardcopy format, ENCS approved electronic calculators.

Question 0: (in computing, we often start counting from 0 ...) [25 points]

(a) Convert $(21.23)_4$ into its base-5 representation with up to 4 significant digits after the "base-5 decimal point".

(b) Convert $(57.6875)_{10}$ into its base-6 representation.

(c) Convert $(21)_{16}$ into its base-8 representation.

(d) Convert $(0.0001)_2$ into its base-4 representation.

Question 1: [25 points]

(a) Give the range of integers representable using 6-bit sign-magnitude notation.

(b) Give the range of integers representable using 6-bit two's complement notation.

(c) Perform the operation:

$$\begin{array}{r} (-16) \\ + (+1) \\ \hline = -15 \end{array}$$

using 6-bit two's complement arithmetic. Indicate whether overflow has occurred.

(d) Perform the operation:

$$\begin{array}{r} -32 \\ \times (-1) \\ \hline = +32 \end{array}$$

using 6-bit two's complement multiplication following the "pencil-paper" method using sign extension.

(e) Convert the following IEEE 754 32-bit floating point format number into its equivalent decimal value:

0 1 0 0 0 0 0 0 0 0 0 1 0

Question 2: [25 points]

Consider the hardware shown in Figure 1 consisting of a 4-bit D-type register, two 2-1 multiplexers, and a 4-bit parallel adder (with one of the adder inputs connected to the constant value of "0001").

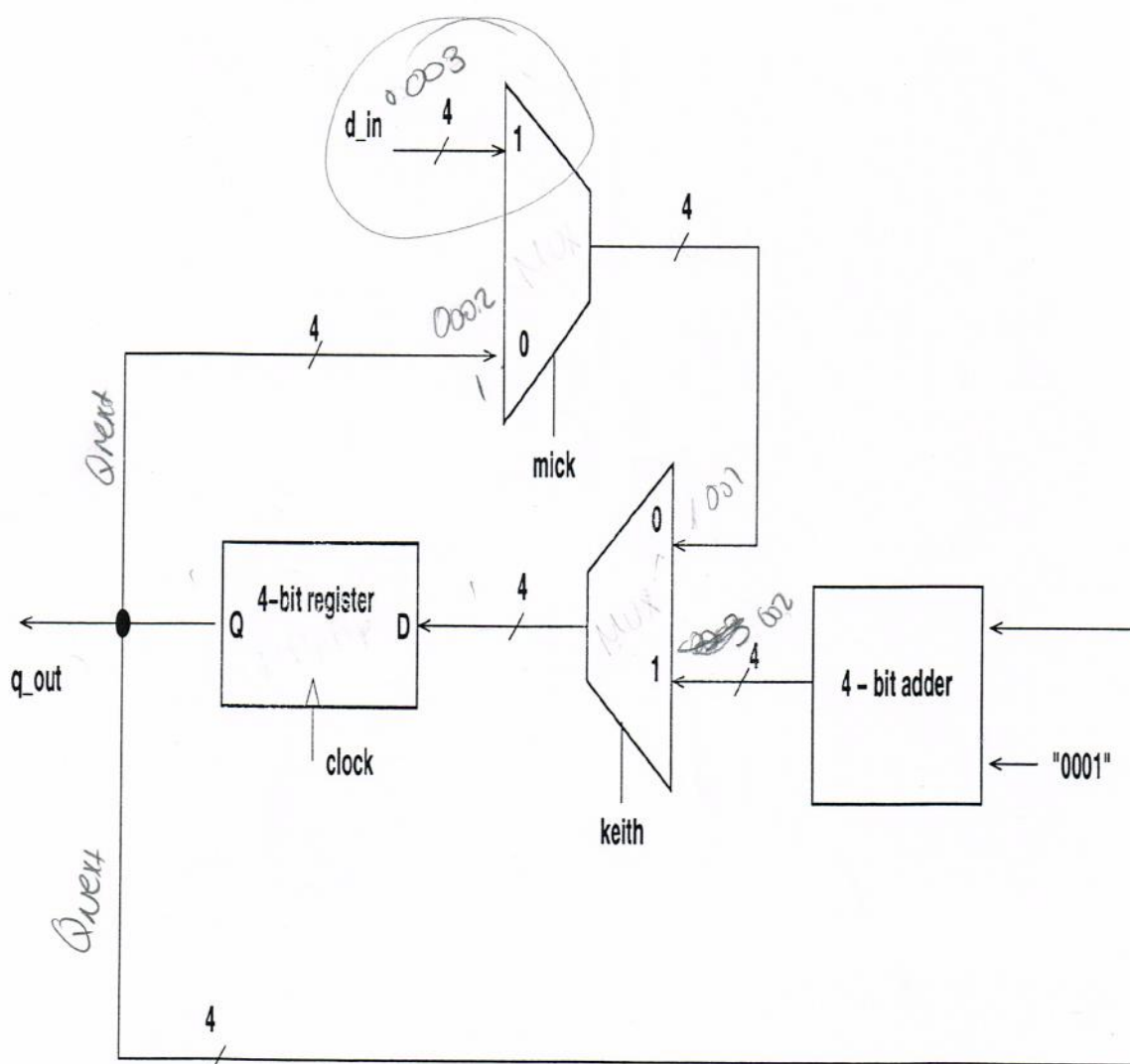


Figure 1: Two muxes, a register, and an adder.

(a) Complete the following table which explains the functionality of the given hardware:

Table 1: Functional Description of hardware in Figure 1

keith	mick	q_out(present)	q_out(next clock)
0	0	q_out	same q_out
0	1	q_out	????
1	0	q_out	????
1	1	q_out	????

(b) Explain in words the functionality of this circuit. Express your answer in a manner similar to:

"This hardware organization is a 4-bit register capable of being loaded at the next rising clock edge with the two's complement of the value presently stored within the register when the signal keith = '1' and mick = '0', or the register may be cleared to "0000" when keith = '0' and mick = '1'."

Of course, the hardware performs something completely different. The above is given merely as an example of how you should express your answer.

(c) Complete the timing diagram given on the last page of this exam. **You may remove the last page and insert it into your answer booklet. WRITE YOUR NAME AND ID NUMBER IN THE SPACE PROVIDED ON THE LAST PAGE.** You may assume 0 delay for the 4-bit register. Indicate the value stored in the 4-bit register (qout) between the lines labelled START and END.

Question 3: [25 points]

A digital logic circuit with output F and three inputs A,B, and C is specified with the following truth table:


Table 2: Truth Table for Question 3

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0

Table 2: Truth Table for Question 3

A	B	C	F
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 (a) Explain in words why the grouping of 1's in the following K-map is not a valid grouping.



(b) Properly minimize F using a Karnaugh map.